

Voting Machine Project

1) Button Control Validity

```
module button_control_VALIDITY(  
    input clk, reset, button,  
    output reg valid_vote);  
  
    //counter for valid_vote//  
    reg [31:0] counter;  
    always@(posedge clk)  
        begin  
            if(reset)  
                counter <= 0;  
            else  
                begin  
                    if(button & counter < 11)  
                        counter <= counter + 1;  
                    else if(!button)  
                        counter <= 0;  
                end  
            end  
        end  
end
```

```
    //valid vote logic//  
    always@(posedge clk)  
        begin  
            if(reset)  
                valid_vote<=1'b0;  
            else  
                begin  
                    if(counter==10)  
                        valid_vote<=1'b1;  
                    else  
                        valid_vote<=1'b0;  
                    end  
                end  
            end  
        end  
endmodule
```

2) Vote Logger

```
module vote_logger(  
    input clk, reset, mode, cand1_vote_valid, cand2_vote_valid, cand3_vote_valid, cand4_vote_valid,  
    output reg [31:0] cand1_vote_rcvd, cand2_vote_rcvd, cand3_vote_rcvd, cand4_vote_rcvd);  
  
    always@(posedge clk)  
    begin  
        if(reset)  
        begin  
            cand1_vote_rcvd<=0;  
            cand2_vote_rcvd<=0;  
            cand3_vote_rcvd<=0;  
            cand4_vote_rcvd<=0;  
        end  
        else if(mode==0) begin  
            if(cand1_vote_valid)  
                cand1_vote_rcvd<=cand1_vote_rcvd+1;  
            else if(cand2_vote_valid)  
                cand2_vote_rcvd<=cand2_vote_rcvd+1;  
            else if(cand3_vote_valid)  
                cand3_vote_rcvd<=cand3_vote_rcvd+1;  
            else if(cand4_vote_valid)  
                cand4_vote_rcvd<=cand4_vote_rcvd+1;  
        end  
    end  
endmodule
```

Activate Windows
Go to Settings to activate Windows.

3) LED Control

```
module led_ctrl(  
    input clk, reset, mode, valid_vote_casted,  
    input [7:0] cand1_vote, cand2_vote, cand3_vote, cand4_vote,  
    input cand1_button_press, cand2_button_press, cand3_button_press, cand4_button_press,  
    output reg [7:0] LEDs);  
  
    reg [31:0] counter;  
  
    always@(posedge clk)  
    begin  
        if(reset)  
            counter<=0;  
        else if(valid_vote_casted)  
            counter<=counter+1;  
        else if(counter!=0 & counter<10)  
            counter<=counter+1;  
        else  
            counter<=0;  
    end  
end
```

```

always@(posedge clk)
begin
  if(reset)
    LEDs <= 0;
  else
    begin
      if(mode==0 & counter<10)
        LEDs <= 8'hFF;
      else if(mode==0) //voting mode
        LEDs <= 0;
      else if(mode==1) //result mode
        begin
          if(cand1_button_press)
            LEDs<=cand1_vote;
          else if(cand2_button_press)
            LEDs<=cand2_vote;
          else if(cand3_button_press)
            LEDs<=cand3_vote;
          else if(cand4_button_press)
            LEDs<=cand4_vote;
        end
      end
    end
end
endmodule

```

Activate Windows
Go to Settings to activate Windows.

4) Top Module

```

module voting_machine(
  input clk, reset, mode, cand1_button, cand2_button, cand3_button, cand4_button,
  output [7:0] LEDs);

  wire valid_vote_1, valid_vote_2, valid_vote_3, valid_vote_4;
  wire [7:0] cand1_vote_rcvd, cand2_vote_rcvd, cand3_vote_rcvd, cand4_vote_rcvd;
  wire any_valid_vote;

  button_control_VALIDITY bc1(
    .clk(clk), .reset(reset),
    .button(cand1_button),
    .valid_vote(valid_vote_1)
  );

  button_control_VALIDITY bc2(
    .clk(clk), .reset(reset),
    .button(cand2_button),
    .valid_vote(valid_vote_2)
  );

  button_control_VALIDITY bc3(
    .clk(clk), .reset(reset),
    .button(cand3_button),
    .valid_vote(valid_vote_3)
  );

```

Acti
Go to

```

button_control_VALIDITY bc4(
    .clk(clk), .reset(reset),
    .button(cand4_button),
    .valid_vote(valid_vote_4)
);

assign any_valid_vote = valid_vote_1 | valid_vote_2 | valid_vote_3 | valid_vote_4;

vote_logger VL(
    .clk(clk), .reset(reset), .mode(mode),
    .cand1_vote_valid(valid_vote_1),
    .cand2_vote_valid(valid_vote_2),
    .cand3_vote_valid(valid_vote_3),
    .cand4_vote_valid(valid_vote_4),
    .cand1_vote_rcvd(cand1_vote_rcvd),
    .cand2_vote_rcvd(cand2_vote_rcvd),
    .cand3_vote_rcvd(cand3_vote_rcvd),
    .cand4_vote_rcvd(cand4_vote_rcvd)
);

```

```

led_ctrl LC(
    .clk(clk), .reset(reset), .mode(mode),
    .valid_vote_casted(any_valid_vote),
    .cand1_vote(cand1_vote_rcvd),
    .cand2_vote(cand2_vote_rcvd),
    .cand3_vote(cand3_vote_rcvd),
    .cand4_vote(cand4_vote_rcvd),
    .cand1_button_press(valid_vote_1),
    .cand2_button_press(valid_vote_2),
    .cand3_button_press(valid_vote_3),
    .cand4_button_press(valid_vote_4),
    .LEDs(LEDs)
);
endmodule

```

Testbench

```

module tb_voting_machine;

reg clk, reset, mode;
reg button1 ,button2, button3, button4;
wire [7:0] LEDs;

voting_machine DUT(.clk(clk), .reset(reset), .mode(mode),
    .cand1_button(button1), .cand2_button(button2), .cand3_button(button3), .cand4_button(button4),
    .LEDs(LEDs));

initial begin
    clk=0;
    forever #5 clk=~clk;
end

initial begin
    // Initialize Inputs
    reset = 1; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
    // Wait 100 ns for global reset to finish
    #100;

    // Add stimulus here

```

```

#5 reset = 0; mode = 0; button1 = 1; button2 = 0; button3 = 0; button4 = 0;
#10 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 1; button2 = 0; button3 = 0; button4 = 0;
#200 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#10 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;

#5 reset = 0; mode = 0; button1 = 0; button2 = 1; button3 = 0; button4 = 0;
#200 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#10 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;

#5 reset = 0; mode = 0; button1 = 0; button2 = 1; button3 = 1; button4 = 0;
#200 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#10 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;


#5 reset = 0; mode = 1; button1 = 0; button2 = 1; button3 = 0; button4 = 0;
#200 reset = 0; mode = 1; button1 = 0; button2 = 0; button3 = 1; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#10 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;

#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 1; button4 = 0;
#200 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#10 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;
#5 reset = 0; mode = 0; button1 = 0; button2 = 0; button3 = 0; button4 = 0;

$finish;
end
initial
$monitor($time, "mode = %b, button1 = %b, button2 = %b, button3 = %b, button4 = %b, led = %d",
mode, button1, button2, button3, button4, LEDs);
endmodule

```

RTL Viewer

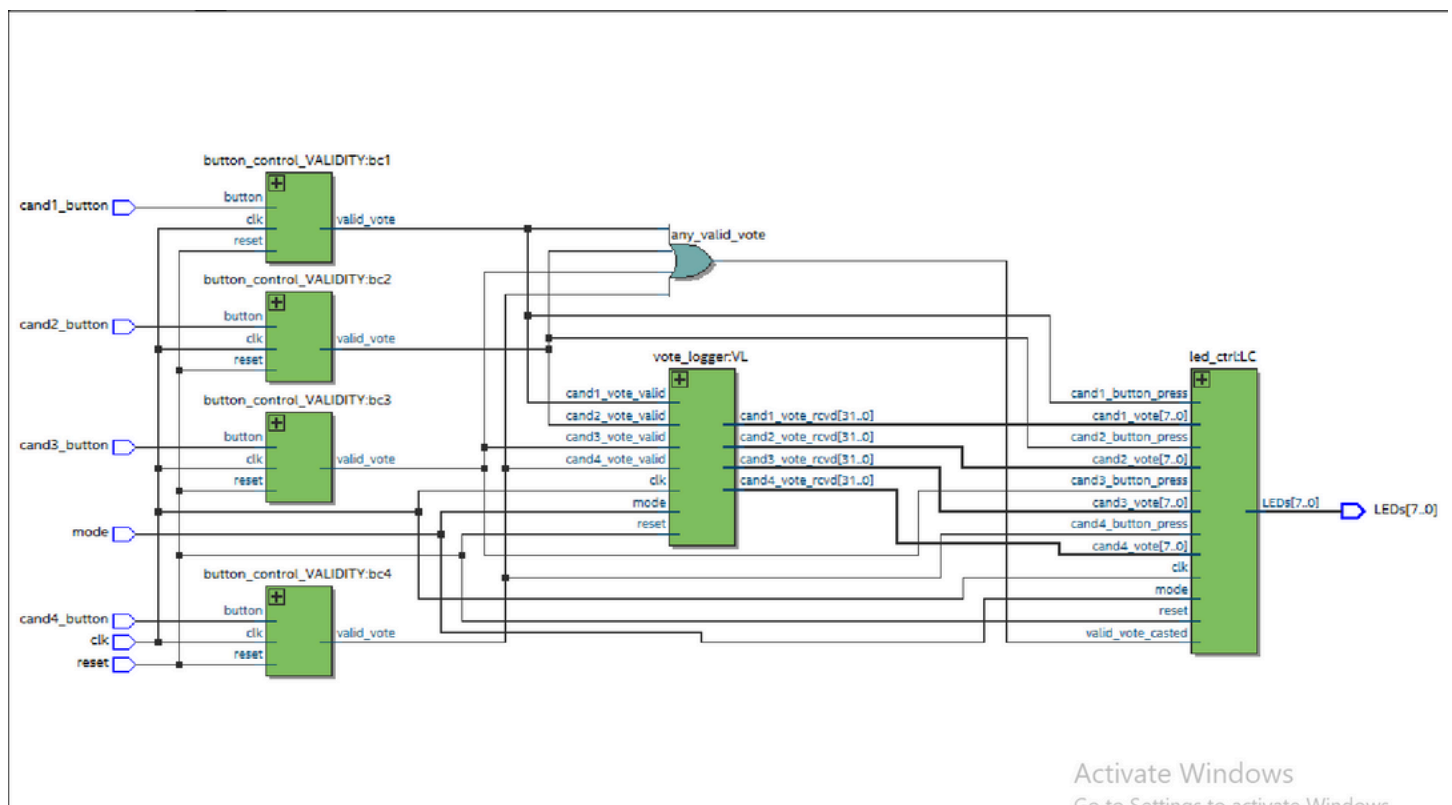

WAVEFORM

